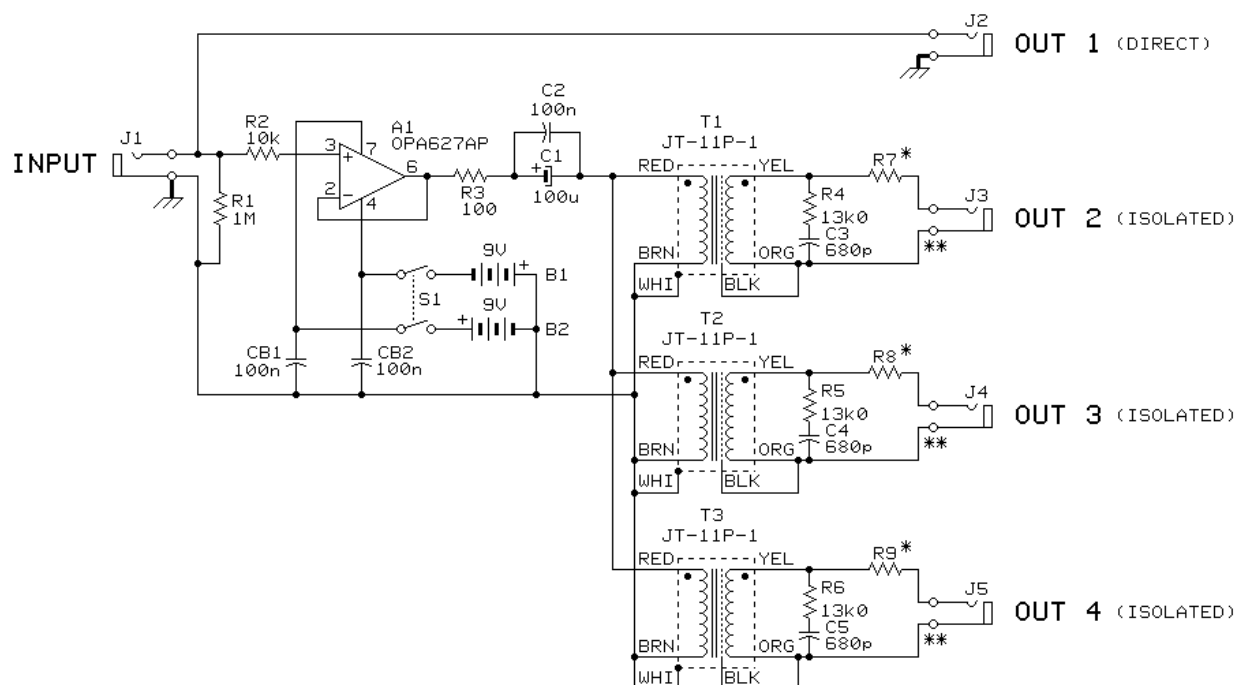


4 WAY ACTIVE GUITAR "SPLITTER" or DISTRIBUTION AMPLIFIER



A LOWER COST OP-AMP, SUCH AS THE LF356N, MAY BE SUBSTITUTED FOR A1. ITS SLIGHTLY HIGHER NOISE (HISS) WILL BE INSIGNIFICANT UNLESS THE DC RESISTANCE OF THE PICKUP IS UNDER 3 kΩ,

*R7, R8, AND R9 CAN RANGE IN VALUE UP TO 50 kΩ OR CAN BE 50 kΩ POTENTIOMETERS. THEY WILL PRODUCE TREBLE ROLL OFF SIMILAR TO THE DIRECT OUTPUT, WITH HIGHER VALUES PRODUCING THE MOST ROLL OFF.

** J3, J4, AND J5 MOUNTING MUST INSULATE THEM FROM THE CHASSIS.

© COPYRIGHT 1996, JENSEN TRANSFORMERS, INC.

jensen	AS014
	01/11/96
7135 HAYVENHURST AVE. VAN NUYS, CALIFORNIA 91406 (818) 374-5857	